

g.g.

$$T(j\omega) = -j\omega R_2 C_1 \cdot \frac{1}{1+j\omega R_1 C_1} \cdot \frac{1}{1+j\omega R_2 C_2}$$

$$T(f) = - \left( \frac{f}{f_3} \right) \cdot \frac{1}{1+jf/f_1} \cdot \frac{1}{1+jf/f_2}$$

$f_1 = 10 \text{ kHz}$      $f_2 = 2 \text{ kHz}$      $f_3 = 34 \text{ Hz}$

