

4.1

$$\left. \begin{array}{l} V_3 = -g V_2 \frac{R_L}{R_L + R_S} \\ V_2 = -g V_1 \frac{R_e}{R_e + R_S} \end{array} \right\}$$

$$P_S = \frac{V_3^2}{R_L}$$

$$P_e = \frac{V_1^2}{R_e}$$

$$G_P = \frac{P_S}{P_e} = \frac{V_3^2}{R_L} \cdot \frac{R_e}{V_1^2} = \frac{R_e}{R_L} \left(\frac{V_3}{V_1} \right)^2$$

donc $P_2 = \frac{V_3^2}{R_L}$

$$P_1 = \frac{V_1^2}{R_e}$$

$$\text{et } V_1 = e \cdot \frac{R_e}{R_e + R}$$

$$G_P = K \frac{\frac{R_e^3}{(R_e + R_S)^2}}{e^2} \quad \text{si } R_e \gg G_P \approx$$

