



Bei den noeds : $i_1 = i_2 + i_3$ $U = Z_i \Rightarrow i = Y_U$

$$V_{AP} \cdot Y_1 = V_{PB} Y_2 + V_{PC} Y_3$$

$$(U_A - V_p) Y_1 = (V_p - V_B) Y_2 + (V_p - V_C) Y_3$$

$$V_p (Y_1 + Y_2 + Y_3) = V_A Y_1 + V_B Y_2 + V_C Y_3$$

$$V_p = \frac{V_A Y_1 + V_B Y_2 + V_C Y_3}{Y_1 + Y_2 + Y_3}$$