

8.5

$$\begin{cases} v^+ = 0 \\ v^- = \frac{v_e / Z_1 + v_s / R}{1/Z_1 + 1/R} \end{cases} \quad Z_2 = R + \frac{1}{j\omega C} = \frac{1 + j\omega RC}{j\omega C}$$

$$v^- = v^+ = 0 \Rightarrow \frac{v_e}{Z_1} + \frac{v_s}{R} = 0$$

$$\frac{v_e}{Z_1} = -\frac{v_s}{R} \Rightarrow \boxed{\frac{v_s}{v_e} = -\frac{R}{Z_1}}$$

$$\frac{v_s}{v_e} = -\frac{R}{\frac{1 + j\omega RC}{j\omega C}} = -\frac{j\omega RC}{1 + j\omega RC}$$

$$\boxed{\frac{v_s}{v_e}} = - \frac{j\omega / \rho_1}{1 + j\omega / \rho_2} = - \left( \frac{j\omega / \rho_1}{\omega} \right) \cdot \left( \frac{1}{1 + j\omega / \rho_2} \right)$$

$$f_1 = \frac{1}{2\pi RC} = 1.6 \text{ kHz} \quad f_2 = \frac{1}{2\pi RC} = 16 \text{ kHz}$$

