

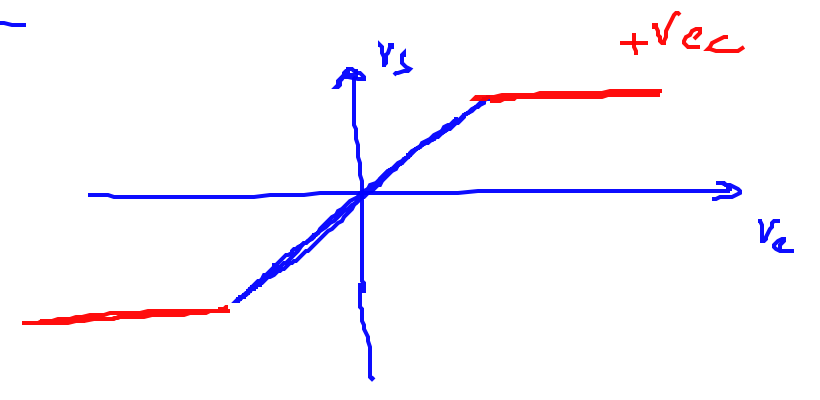


Seq 11

Fcts non linéaires de l'ampli op.

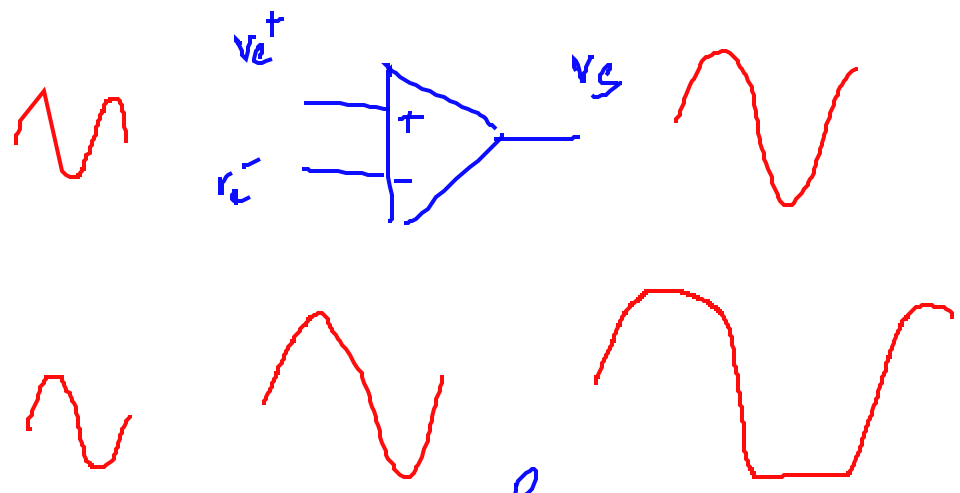

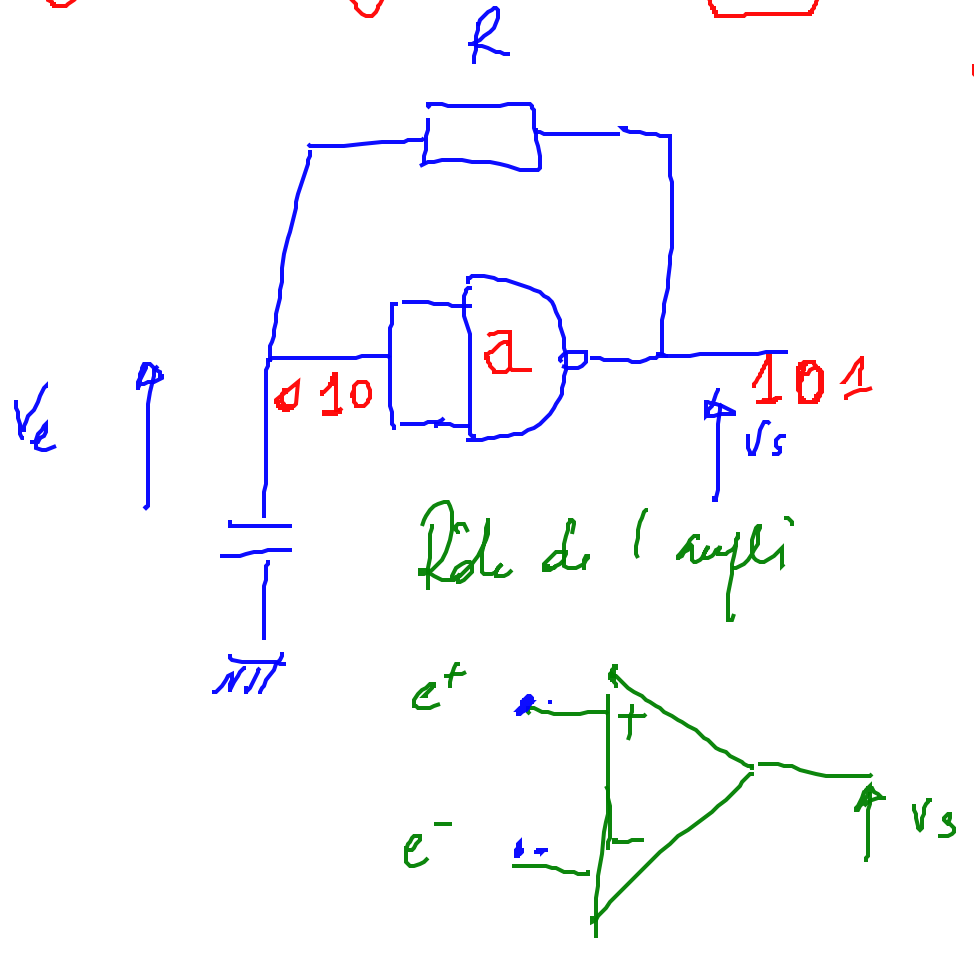astables.
monostable,
circuits oscillants entre $-V_{cc}$ et $+V_{cc}$.



si $e^+ > e^- \rightarrow v_s = +V_{cc}$
 si $e^+ < e^- \rightarrow v_s = -V_{cc}$